




# Circuits and Code

CS 2130: Computer Systems and Organization 1  
February 2, 2026

# Announcements



- Homework 1 due tonight
- Homework 2 available today, due next Monday

# Building a Counter

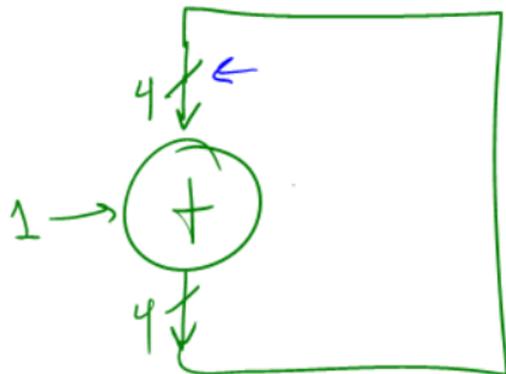


# Gate Delay

What happens when I change my input?

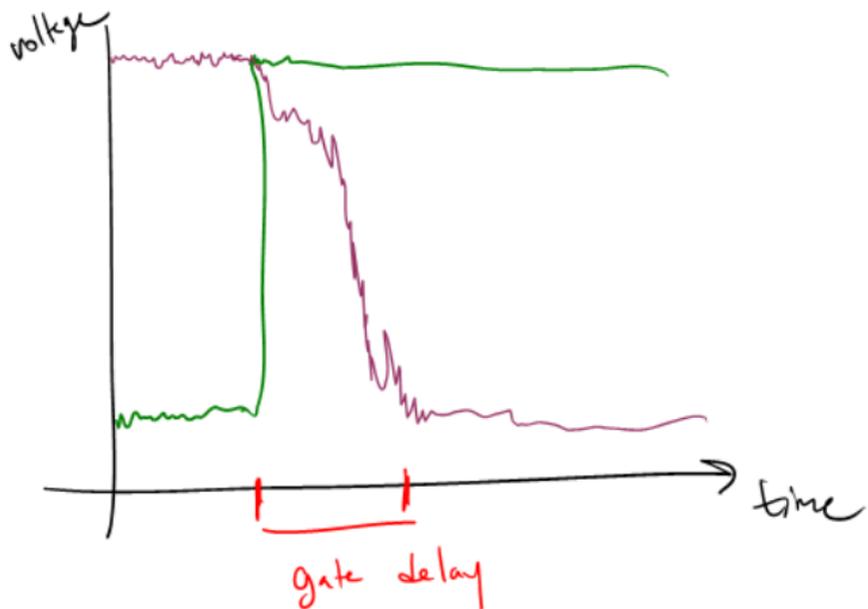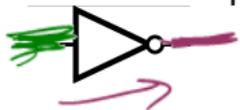




# Building a Counter - Waiting

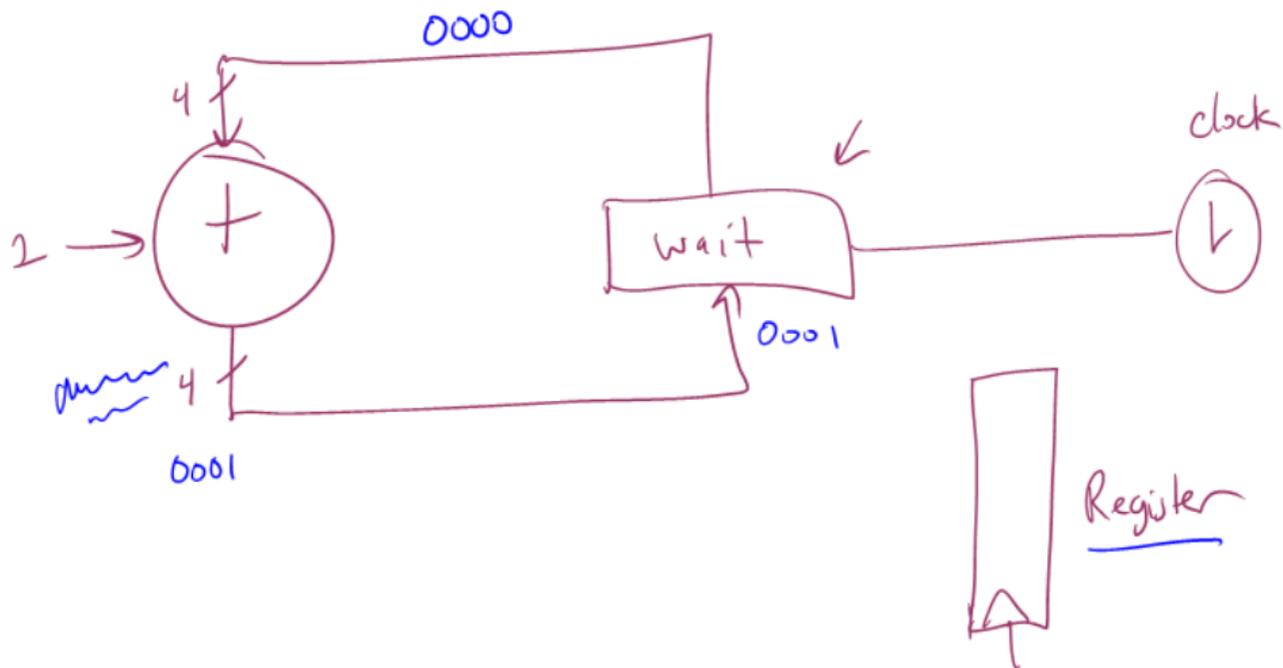


# 1-bit Register Circuit

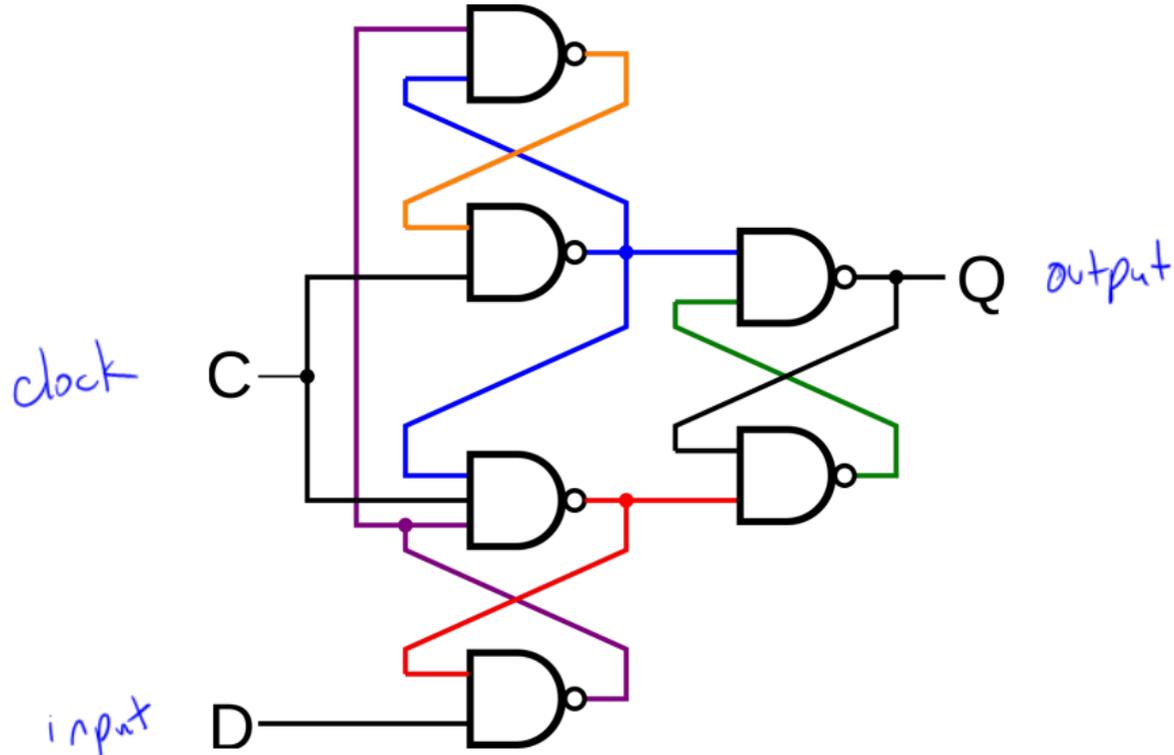





# 1-bit Register Circuit

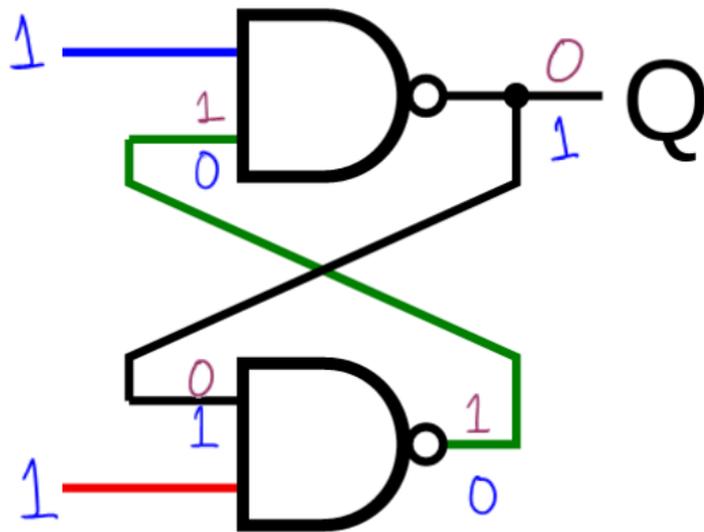


# 1-bit Register Circuit

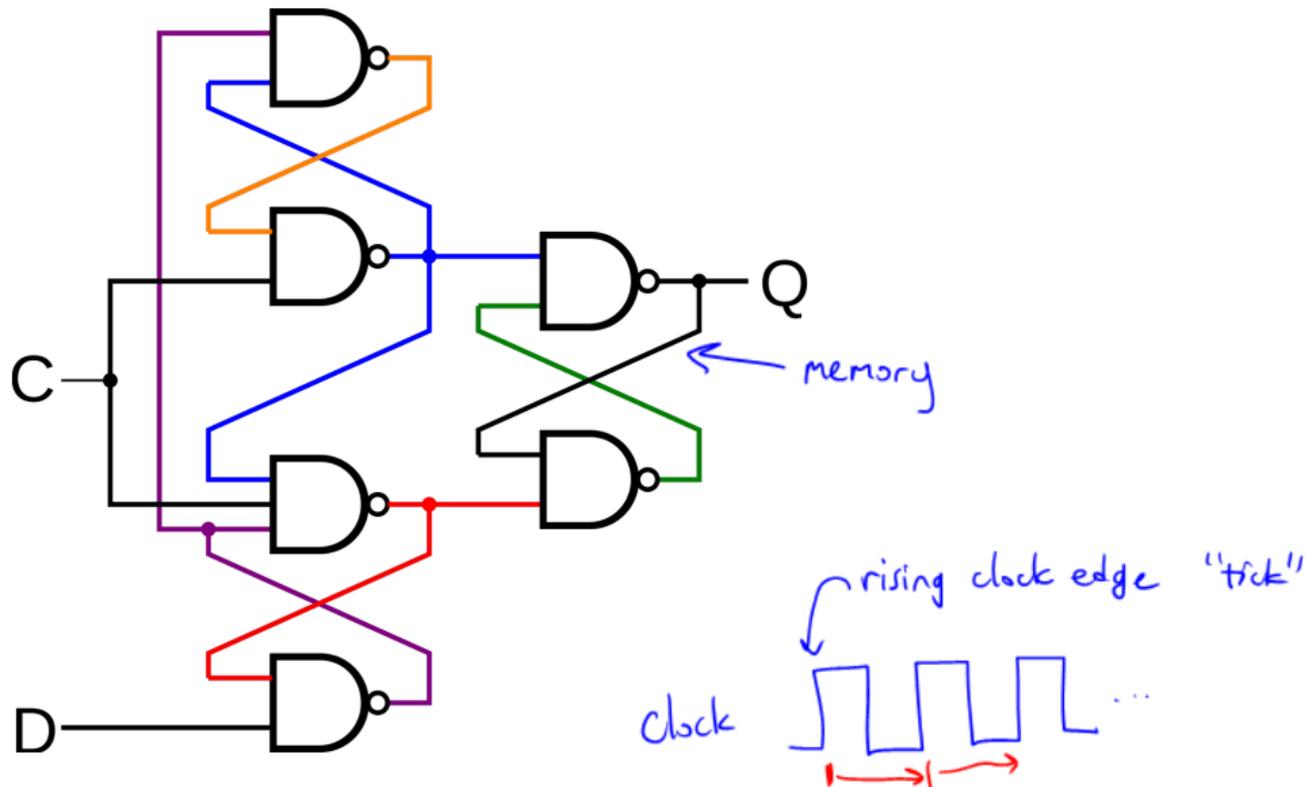


# Building a Counter

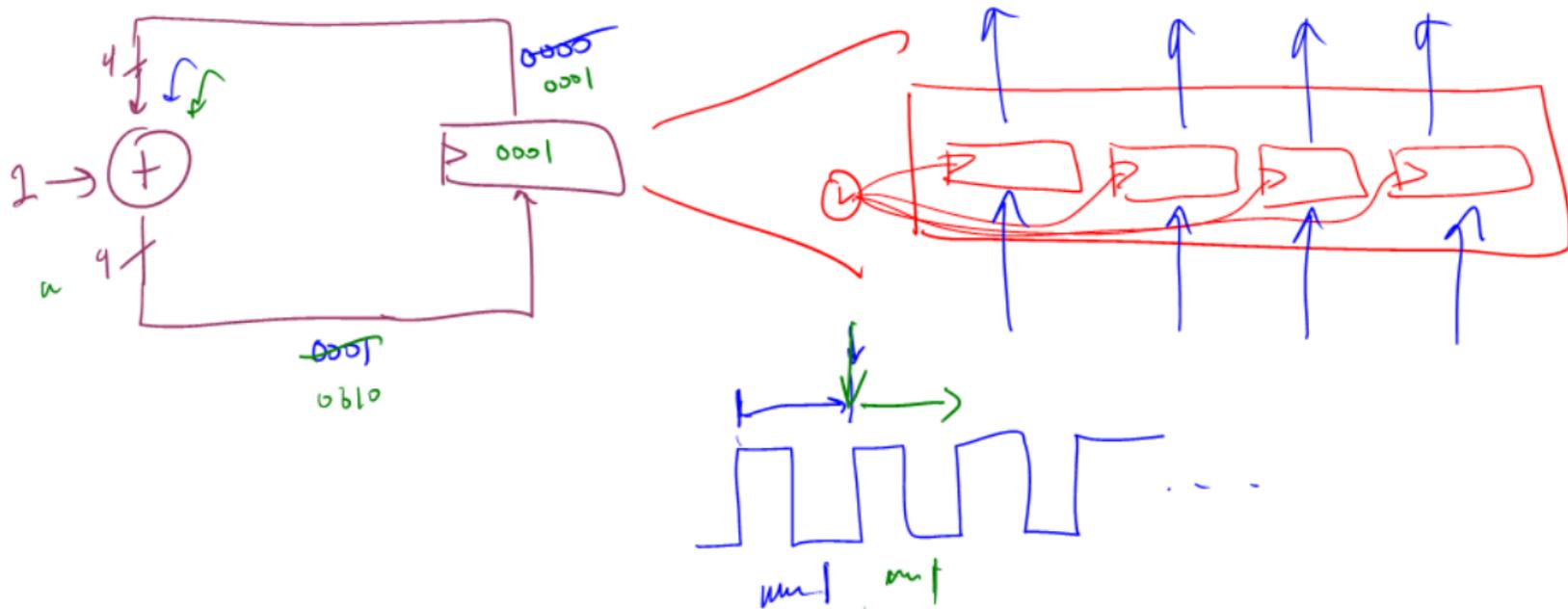

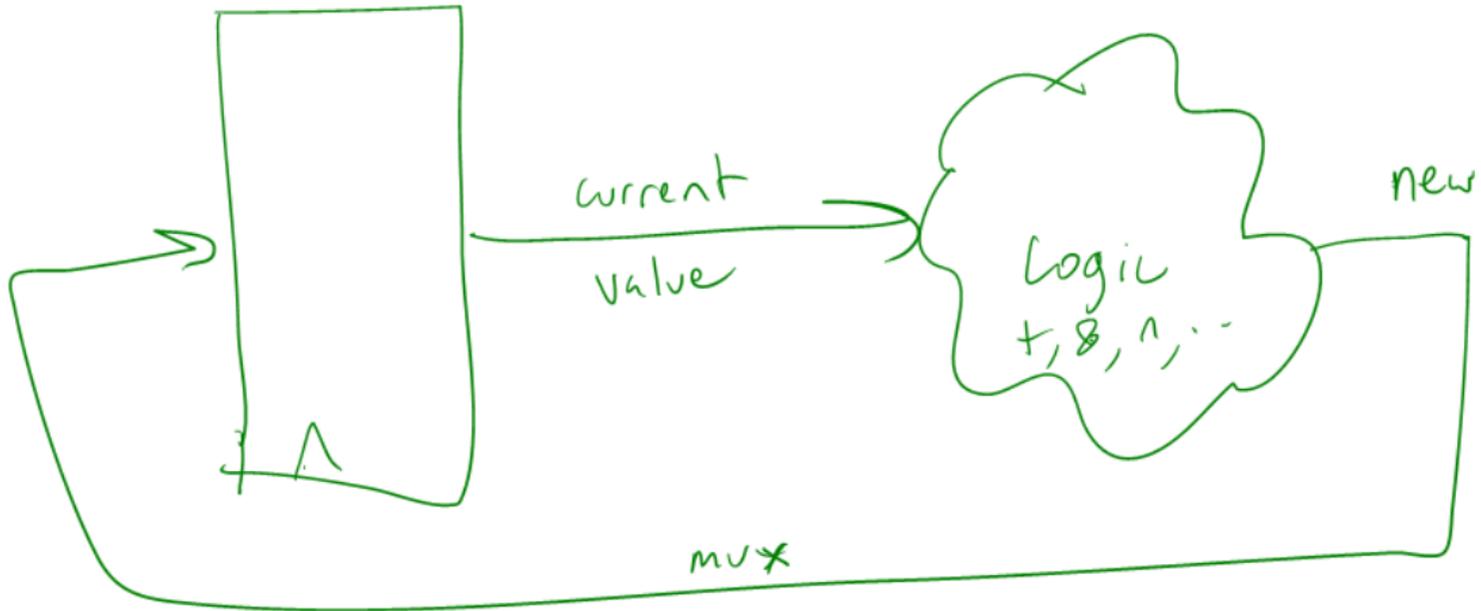


# Another Circuit

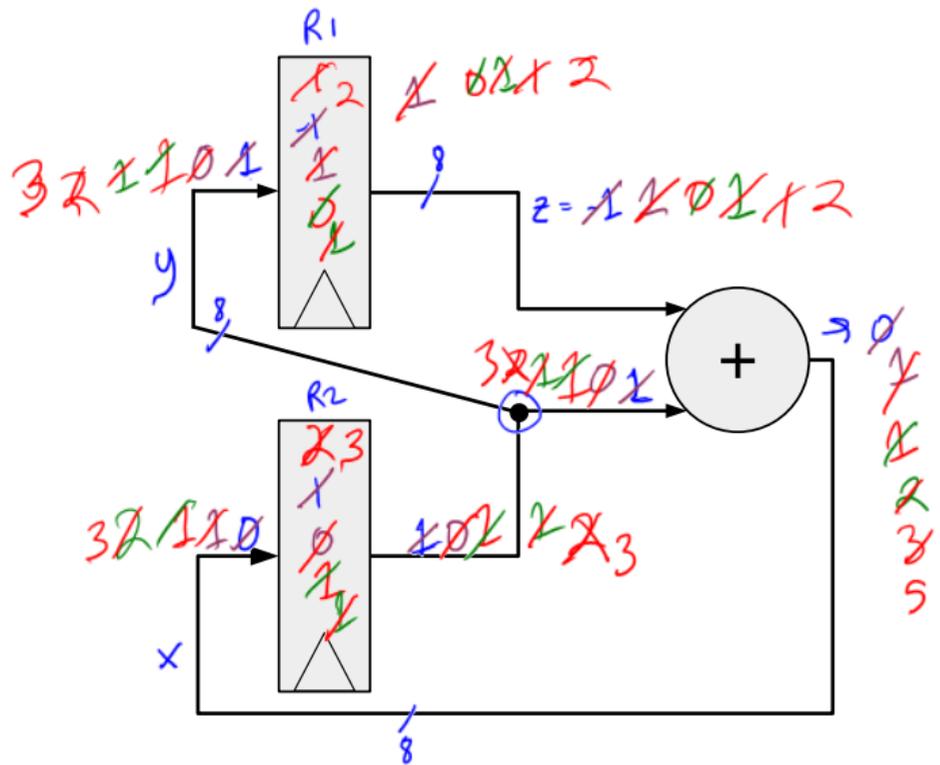

tick	x	y	$R_1$	$R_2$
0	0	1	-1	1
1	1	0	1	0
2	2	1	0	1
3	2	1	1	1
4	3	2	1	2
5	5	3	2	3

# Another Circuit

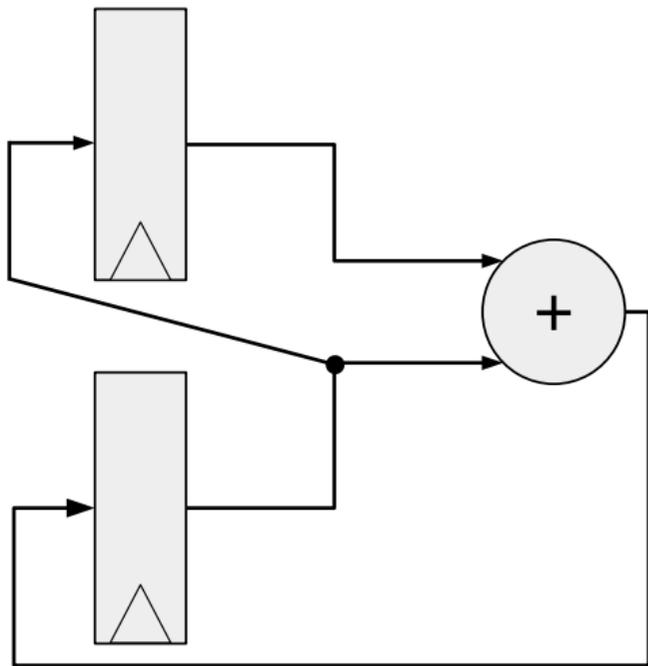

# Common Model in Computers

# Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know:  $\&$ ,  $|$ ,  $\wedge$ ,  $\sim$
- Operations we can build from gates:  $+$ ,  $-$
- Others we can build:  $*$

$$\begin{array}{r} 1010 \\ * 1101 \\ \hline 1010 \\ 0000 \\ 101000 \\ + 101000 \\ \hline \end{array} \quad \begin{array}{l} \& \\ \ll \end{array}$$

# Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know:  $\&$ ,  $|$ ,  $\wedge$ ,  $\sim$
- Operations we can build from gates:  $+$ ,  $-$
- Others we can build:
- Ternary operator:  $?$  :

$z = (a == b) ? x : y$

# Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex:  $z = x * y$

# Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex:  $z = x * y$
- What about the following?  
 $x = 1$   
 $x = 0$

# Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex:  $z = x * y$
- What about the following?  
 $x = 1$   
 $x = 0$
- **Single assignment:** each variable can only be assigned a value once